
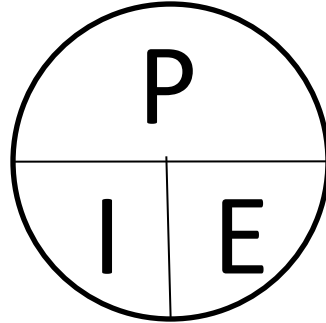

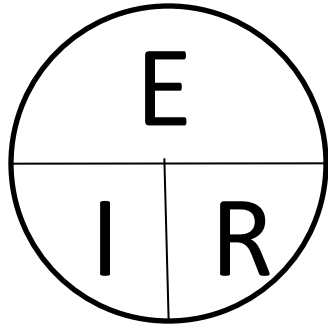
# The Really Important Formulas

By VE3FYN, Warren Paulson  
ver 3.3, 27 February 2012



P = Power (Watts)  
E = Potential Difference (Volts)  
I = Current (Amps)  
R = Resistance (Ohms)

*Ohm's Law*

300 / Frequency (MHz) = Wavelength (M)  
300 / Wavelength (M) = Frequency (MHz)

*Frequency & Wavelength*

Turns ratio =  $\frac{N_p}{N_s}$      $N_p$  = Primary turns    Voltage will vary by the turns ratio.  
 $N_s$  = Secondary turns    Current will vary by the inverse.

*Transformer  
Turns Ratio*

Series Resistance =  $R_1 + R_2 + R_3 \dots$

Parallel  
Resistance =  $\frac{R_1 \times R_2}{R_1 + R_2}$

Inductance is calculated like Resistance  
Capacitance is calculated in reverse


*Series &  
Parallel*

# Other Important Formulas
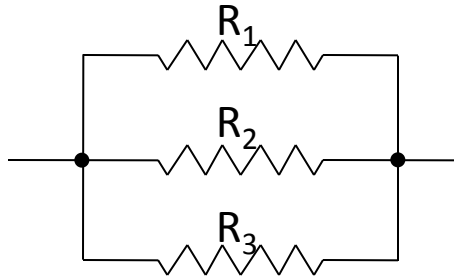
## Series & Parallel (Resistance)



- $R_T = R_1 + R_2 + R_3$
- $I = E / R_T$  → Current is the same, wherever you measure it.
- $E \text{ at } R_x = I_T * R_x$  → Voltage drop is different at each resistor.  
→ Total voltage drop is the sum of  $E_1 + E_2 + E_3$



$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

- $I_x = E / R_x$  → Current is different at each resistor.
- $E_x = E_T$  → Voltage drop is the same, wherever you measure it.

## Frequency and period

$$F = 1 / T \text{ and } T = 1 / F \text{ where 'T' = 1 cycle}$$

## Series & Parallel Resistance (non-math)

If x equal value resistors are in parallel, the total R is the value of one resistor over the number of resistors, or  $R / X$ .

The total resistance in a parallel circuit is always less than that of the smallest resistor.

The total resistance of two equal value resistors is half the value of either resistor.

# Unit Conversions

Name	Symbol	Multiplier	Exponent
Giga	G	X 1 000 000 000	$10^9$
Mega	M	X 1 000 000	$10^6$
Kilo	K	X 1 000	$10^3$
UNIT			
milli	m	/ 1 000	$10^{-3}$
micro	$\mu$	/ 1 000 000	$10^{-6}$
nano	n	/ 1 000 000 000	$10^{-9}$
pico	p	/1 000 000 000 000	$10^{-12}$

# ***Reactance***

## ***Capacitive and Inductive Reactance***

- **Capacitance** ( $C$ ) refers to the physical properties of a capacitor.
- **Inductance** ( $L$ ) refers to the physical properties of an inductor.
- **Reactance** ( $X$ ), measured in ohms, is the opposition to AC current by a capacitor or inductor (or both).
- **Impedance** ( $Z$ ), AC resistance, is reactance plus pure resistance. (See optional formulas for the math.)
- **Capacitive reactance** ( $X_C$ ) is the opposition to AC current flow by a capacitor.
  - It is inversely proportional to frequency.
- **Inductive reactance** ( $X_L$ ) is the opposition to AC current flow by an inductor.
  - It is directly proportional to frequency.

### ***Capacitive Reactance***

$$X_C = \frac{1}{2 \pi f C}$$

### ***Inductive Reactance***

$$X_L = 2 \pi f L$$

# Decibels

Power	Decibel
2	3
4	6
6	8
8	9
10	10
100	20
1000	30

<- Remember this chart, and you know all the decibel conversions you need to know for the exam. Also read the article at <http://www.ve3fyn.ca/nvis/Decibel.htm>

\* A change of 1 dB is generally the minimum a person can detect if it is expected. A change of 3 dB, (doubling or halving the power) is generally the minimum a person can detect if it is not expected.

$\text{dB} = 10\text{Log}(P_2/P_1)$  where 'P' is power       $\text{dB} = 20\text{Log}(E_2/E_1)$  where 'E' is voltage

On your calculator:  $(P_2 \div P_1) \{\text{Log}\} * 10 =$  or  $(E_2 \div E_1) \{\text{Log}\} * 20 =$

dB to Power Ratio on your calculator:  $(\text{dB} \div 10) \{2\text{ndF}\} \{10^x\} =$

## To convert a two-digit decibel to its power ratio:

The first digit tells you the magnitude. The second digit tells you the value.

So, with 36 dB, the '3' tells you it's in the thousands.

The '6' is a power ratio of 4. So 36 dB = 4000 times the power.

# Good Stuff That's Not on the Basic Exam

## Impedance turns ratio

$$\frac{N_p}{N_s} = \sqrt{\frac{Z_p}{Z_s}}$$

Where:  
 $N_p$  = Number of primary turns,  
 $N_s$  = Number of secondary turns,  
 $Z_p$  = Primary impedance,  
 $Z_s$  = Secondary impedance.

## Impedance

$$Z = \sqrt{R^2 + X^2}$$

$Z$  = Impedance (ohms)  
 $R$  = Resistance (ohms)  
 $X$  = Reactance (ohms)

## Resonant Frequency

- Current lags behind voltage in an inductor.
- Current leads voltage in a capacitor.
- At the resonant frequency in an RLC circuit, the inductor and capacitor are in-phase.
- In an RLC series circuit, at resonance, current is maximum.
- In a parallel LC circuit, at resonance current is minimum.

**Resonance**  $f_r = \frac{1}{2\pi\sqrt{LC}}$

# ***More Good Stuff That's Not on the Basic Exam***

## ***Q of Tuned Circuits***

- “Q” refers to the sharpness of the response curve of a tuned circuit.
- It is the ratio between  $X_L$  and R.
- Note that Q is frequency sensitive, as  $X_L$  varies with frequency.


$$Q = \frac{X_L}{R}$$

- A high Q (50 – 250) indicates a coil with little resistance at RF, and a sharp response curve.
- Capacitors have a very high Q, which is effectively irrelevant.
- In a parallel tuned circuit, Q is impedance over reactance ( $Z / X$ )

$$Q = \frac{Z}{X}$$

# Cut-off Frequencies *(also not on exam)*


## High-Pass Filters

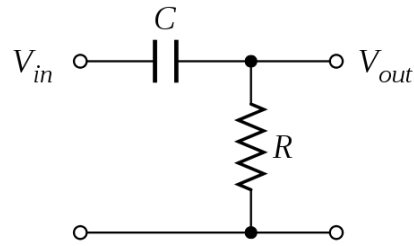

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}$$

- High-pass filters pass high frequencies and reject signals at frequencies below the cut-off point.
- At the cut-off point, output power is  $\frac{1}{2}$  input power.
- $R$  represents the impedance of the circuit in question.
- Higher value capacitors lower the cut-off frequency (frequencies below the cut-off are attenuated).

## Low-Pass Filters

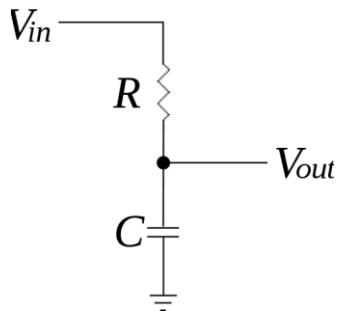


$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}$$

- Low-pass filters pass low frequencies and shunt higher frequencies to ground.
- At the cut-off point, output power is  $\frac{1}{2}$  input power.
- $R$  represents the impedance of the circuit in question.
- Lower value capacitors lower the cut-off frequency (frequencies above the cut-off are attenuated).



## *In Case you Forgot...*

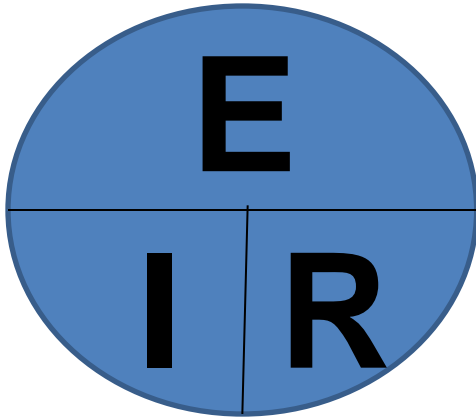


E = voltage (energy)  
measured in volts

I = current  
measured in amperes

R = resistance  
measured in ohms

P = power  
measured in watts

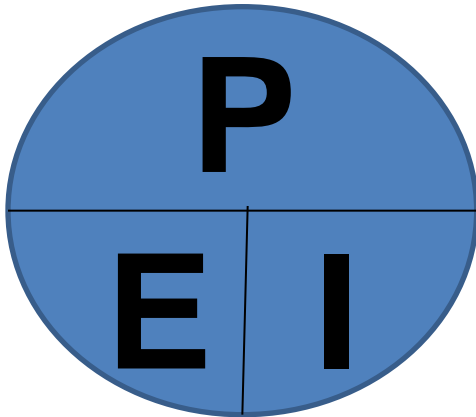

$$E = I * R$$

$$P = E * I$$

$$I = E / R$$

$$E = P / I$$

$$R = E / I$$

$$I = P / E$$

Other formulae may be derived from this. For example:

$$P = E * I$$

$$E = R * I \quad \text{Therefore, } P = R * I * I, \text{ or } P = R * I^2$$